

## 1(a). Kirchhoff's Voltage Law (K.V.L.) and Kirchhoff's Current Law (K.C.L.)

### Kirchhoff's Voltage Law (K.V.L.)

Sum of the voltage in any closed loop must be zero considering same sign convention.

#### Sign Convention:


Lets consider that voltage is positive if we move from plus to minus then voltage is negative if we move from minus to plus. We can consider otherwise also.

Lets apply KVL in single loop network as shown in figure.

$$-V + IR + IR_L = 0 \text{ or } +V - IR - IR_L = 0$$

$$\Rightarrow I = \frac{V}{R + R_L} = \frac{V}{R_{eq,12}}$$
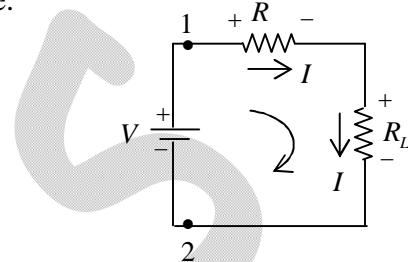
$$\Rightarrow R_{eq,12} = R + R_L \text{ (Series equivalent of resistance)}$$




#### Voltage Division Rule

$$\text{Voltage drop across } R \text{ is } V_R = IR = \frac{VR}{R + R_L}$$

$$\text{Voltage drop across } R_L \text{ is } V_{R_L} = IR_L = \frac{VR_L}{R + R_L}$$

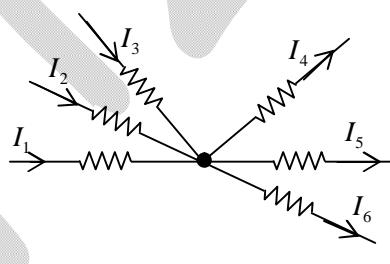
### Kirchhoff's Current Law (K.C.L.)

At any node sum of incoming current is equal to sum of outgoing current.



$$\text{Thus } I_1 + I_2 + I_3 = I_4 + I_5 + I_6$$

## Current Division Rule

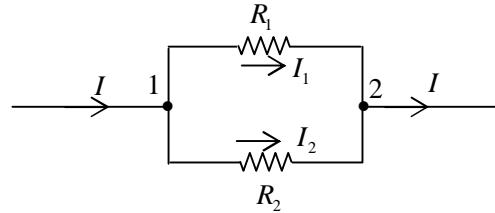

According to KCL at node 1 and 2:  $I = I_1 + I_2 \dots (i)$

Since parallel voltages are equal:  $V_{12} = V = I_1 R_1 = I_2 R_2 \dots (ii)$

Solve equation (i) and (ii) for  $I_1$  and  $I_2$ :

$$I_1 = \frac{R_2}{R_1 + R_2} I \text{ and } I_2 = \frac{R_1}{R_1 + R_2} I$$


$$\text{Then } V_{12} = V = I_1 R_1 = I_2 R_2 = I \frac{R_1 R_2}{R_1 + R_2} = I R_{eq,12}$$

$$\Rightarrow R_{eq,12} = \frac{R_1 R_2}{R_1 + R_2} \text{ (Parallel equivalent of resistance)}$$
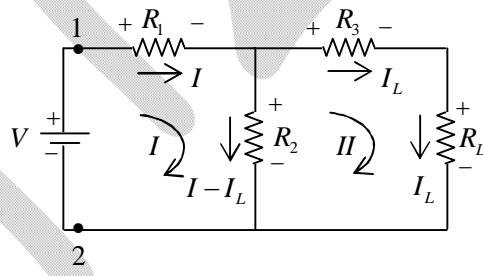
## Two Loop Network

We can find current through each resistance using KVL and current division rule.

Lets apply KVL in two loop network as shown in figure.




$$\text{In loop (I): } -V + IR_1 + (I - I_L)R_2 = 0 \dots (i)$$

$$\text{In loop (II): } I_L R_2 + I_L R_L - (I - I_L)R_2 = 0 \dots (ii)$$

Solve equation (i) and (ii) for  $I$  and  $I_L$ .

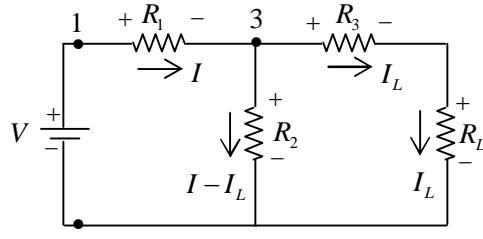Lets apply current division rule in two loop network as shown in figure.



$$\text{Current through } R_1 \text{ is } I = \frac{V}{R_{eq,12}} \text{ where } R_{eq,12} = R_1 + \frac{R_2(R_3 + R_L)}{R_2 + (R_3 + R_L)}$$

Lets apply current division rule at node 3:

$$I_L = \frac{R_2}{R_2 + (R_3 + R_L)} I \quad \text{and} \quad I - I_L = \frac{(R_3 + R_L)}{R_2 + (R_3 + R_L)} I$$

**Example:** Find current across each element in the circuit shown in figure below.

(a) Using current division rule

(b) Using KVL

**Solution:**

$$(a) \text{ Current } I = \frac{12}{3 + \frac{6 \times 14}{6+14}} = \frac{5}{3} A$$

$$I_1 = \frac{6}{6+(7+7)} \times \frac{5}{3} = \frac{1}{2} A$$

$$I_2 = \frac{(7+7)}{6+(7+7)} \times \frac{5}{3} = \frac{7}{6} A$$

(b) Apply KVL in Loop I

$$-12 + 3(I_1 + I_2) + 6I_2 = 0 \Rightarrow 3I_1 + 9I_2 = 12$$

Apply KVL in Loop II

$$7I_1 + 7I_2 - 6I_2 = 0 \Rightarrow 7I_1 = 3I_2$$

Solving above equations, we get  $I_1 = \frac{1}{2} A$  and  $I_2 = \frac{7}{6} A$

